

This question paper contains 8 printed pages]

HPAS (M)—2015

ELECTRICAL ENGINEERING

Paper I

Time : 3 Hours

Maximum Marks : 150

Note :— Attempt Five questions in all, taking at least one from each part, but Question No. 1 is compulsory.

Part A

1. (a) For the pass-band filter shown in Fig. 1.

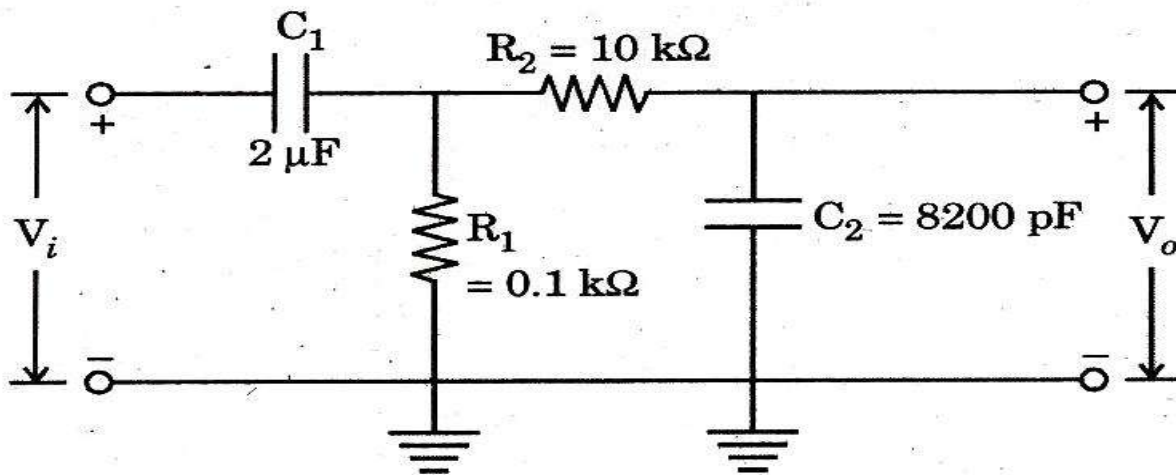


Fig. 1

P.T.O.

- (i) Sketch the frequency response of $A_V = \frac{V_o}{V_i}$ against a log-scale extending from 10 Hz to 10 kHz.
- (ii) What are the bandwidth and the center frequency ?
- (b) Using superposition, find the voltage V_2 for the network in Fig. 2.

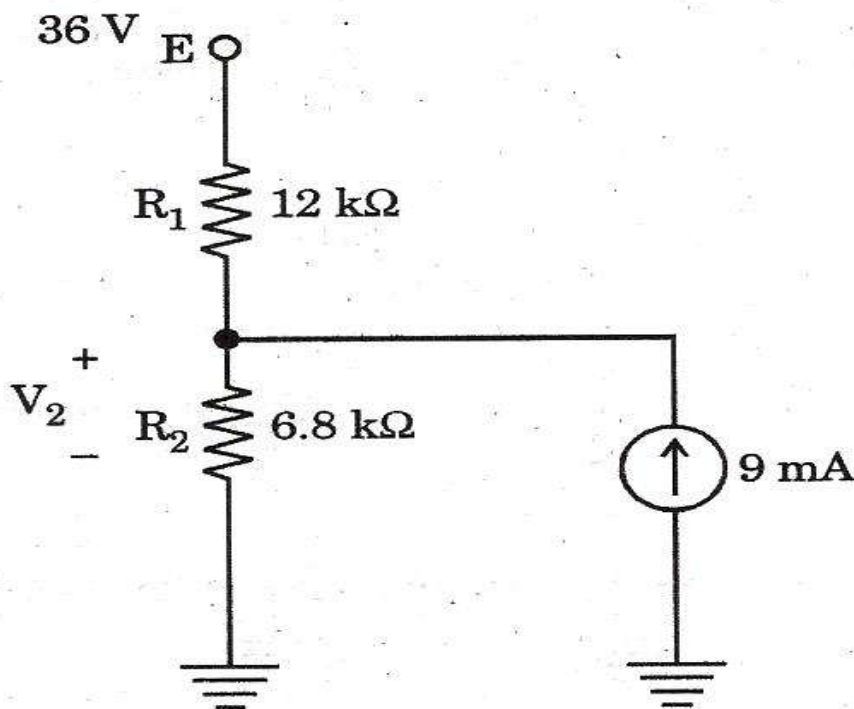


Fig. 2

2. (a) Sketch the following Fourier series expansion :

$$v = 2 + 1 \cos \alpha + 2 \sin \alpha.$$

- (b) (i) If

$$y(z) = \frac{0.5(1 - 0.5z^{-1})}{(1 - 0.25z^{-1})(1 - 0.75z^{-1})(1 - z^{-1})},$$

find the steady-state value of $y(n)$ if it exists.

- (ii) Find $x(\infty)$ if $X(z)$ is given by :

$$X(z) = \frac{3z}{(z - 1)(z + 1)}.$$

Part B

3. (a) Given the potential $V = \frac{10}{r^2} \sin \theta \cos \theta$, find the

electric flux density D , at $\left(2, \frac{\pi}{2}, 0\right)$.

- (b) Show that a rectangular wave guide does not support TM_{10} and TM_{01} modes.

(c) A lossless transmission line with $Z_0 = 50 \Omega$ is 30 m long and operates at 2 MHz. The line is terminated with a load $Z_L = (60 + j40) \Omega$.

If $u = 0.6$ C on the line, find :

(i) The reflection coefficient

(ii) The standing wave ratios

(iii) The input impedance.

4. (a) Draw the circuit that can be used to offset current and offset voltage on inverting amplifier and explain its working.

(b) A customer needs an 18 kHz source at $200 V_{\text{rms}}$ for a special lighting application. The waveform should have THD below 5%. The input source is $240 V_{\text{rms}}$ at 60 Hz. Present a design to meet the loads.

Part C

5. (a) Assume switches ABCD of Fig. 3 are 0110.

Compute output voltage.

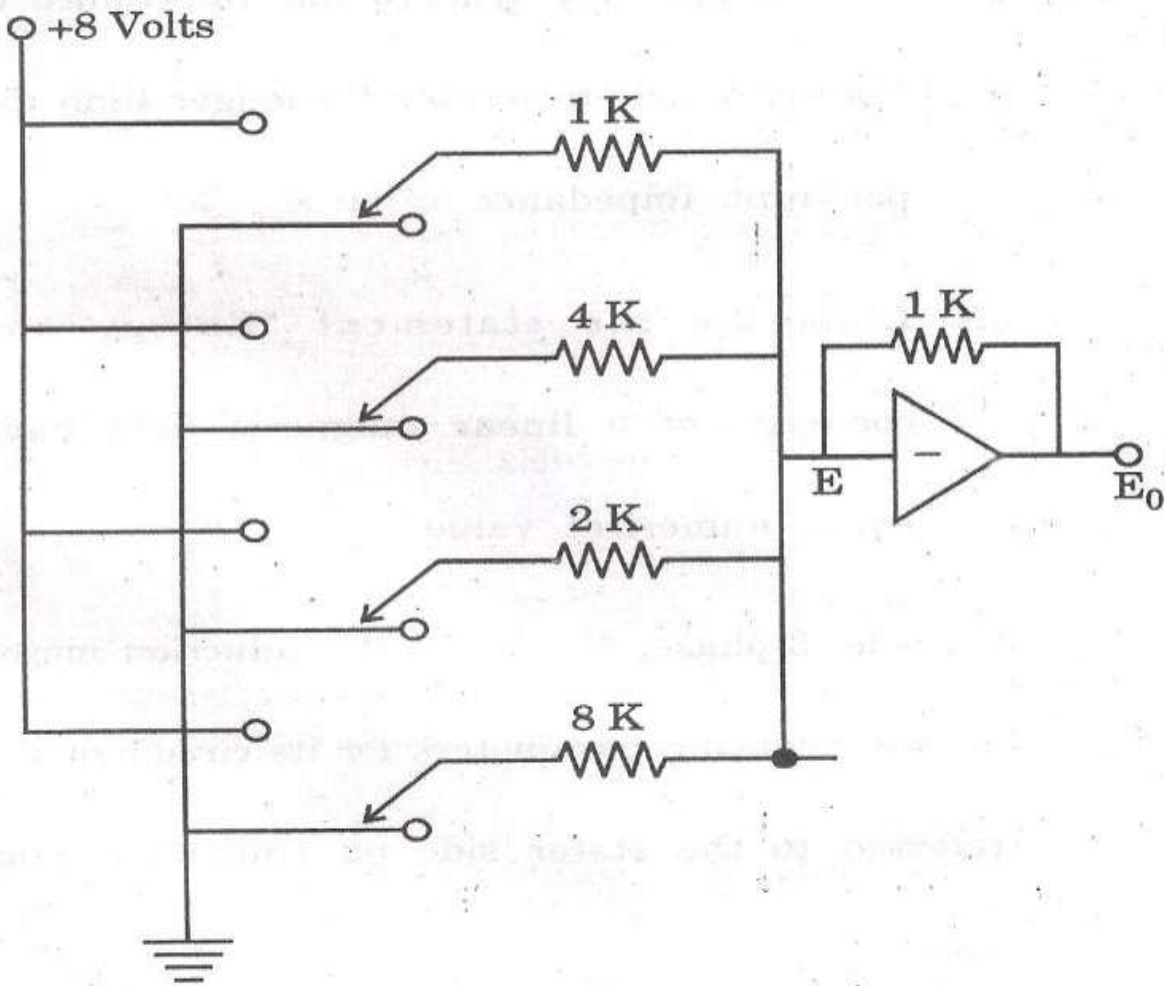


Fig. 3, Summing Network and Amplifier

P.T.O.

- (b) (i) Add 3 and 2 in XS3
- (ii) Add 4318 and 7677 in 8421
- (iii) Convert a binary 1011 to gray code.

6. (a) (i) Why is per unit synchronous impedance of a synchronous generator far longer than the per unit impedance of a X_{er} ?

(ii) Elaborate the statement "Energy and coenergy of a linear magnetic field have equal numerical value".

(b) A 4-pole, 3-phase, 400 V, 50 Hz induction motor has the following parameters for its circuit model (referred to the stator side on equivalent star basis) :

$$r_1 = 1.1 \Omega, \quad X_1 = 1.15 \Omega$$

$$r'_2 = 0.5 \Omega, \quad X'_2 = 1.1 \Omega$$

$X_m = 35 \Omega$ and rotational losses are 800 W.

For a speed of 1440 rpm, calculate the input current, power factor net mechanical power and torque and efficiency.

Part D

7. (a) Discuss the necessity of equalizing networks when thyristors are operated in series/parallel.

Explain the schemes for :

(i) Series operation

(ii) Parallel operation.

- (b) Describe the application of a static frequency converter feeding an a.c. motor for starting and acceleration purposes.

P.T.O.

8. (a) The power in sidebands can have a maximum of one-third of the total AM signal transmitted power for 100% modulation. Calculate the percentage of power in the sidebands for 10% modulation. How does this justify that AM transmitters should be operated with the modulation as close to 100% as possible ?
- (b) Explain in detail the advantages of FM over AM.