

This question paper contains 8 printed pages]

HPAS (Main)—2011

ELECTRICAL ENGINEERING

Paper I

Time : 3 Hours

Maximum Marks : 150

Note :— Attempt Five questions in all, taking at least one question from each part.

PART A

1. (a) For the circuit shown in Fig. 1, obtain current through $(1 + j)$ Ohm impedance using Norton's Theorem. Also, verify your result using Nodal Analysis.

15

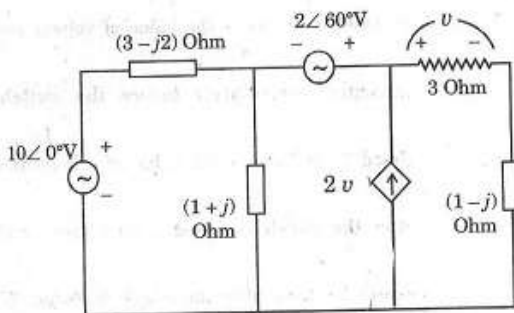


Fig. 1

P.T.O.

- (b) Obtain all the Foster and Cauer realizations of the driving point impedance : 15

$$Z(s) = \frac{s(s^2 + 4)}{(s^2 + 1)(s^2 + 9)}$$

2. (a) State and prove Tellegen's theorem. Also, verify Tellegen's theorem for the circuit in Fig. 1. 15
- (b) The circuit of Fig. 2 has been in the condition shown for a long time. At $t = 0$, the switch is closed. (i) What is the value of voltage across capacitor immediately before the switch is closed ? (ii) What is the value of v immediately after the switch is closed ? Find the complete expression for v after the switch is closed. What is the time constant of transient term ? What

is the final steady state voltage across the capacitor ?

15

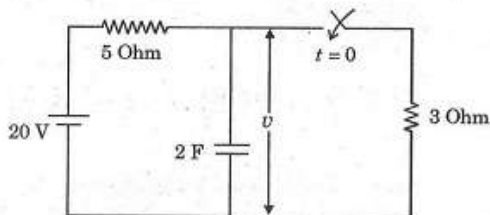


Fig. 2

PART B

3. (a) Derive the expression of capacitance of a parallel plate capacitor using Laplace's Equation. 15
- (b) There exists a boundary between two magnetic materials at $y = 0$, having relative permeabilities $\mu_{r1} = 4$ for region 1 where $y > 0$ and $\mu_{r2} = 6$

P.T.O.

for region 2 where $y < 0$. There exists a surface

current of density $\vec{K} = 60 \hat{a}_x$ A/m at the boundary

$y = 0$. For a field $\vec{B}_1 = 2 \hat{a}_x - 3 \hat{a}_y + \hat{a}_z$ mT in

region 1, find the values of magnetic field intensities

\vec{H}_1 and \vec{H}_2 in two regions. Also, obtain the

magnetic flux density in region 2 (\vec{B}_2). 15

4. (a) Describe in detail, the construction, working and

applications of CRO. 15

- (b) Discuss how inductance and capacitance can be

measured ? Explain in detail. 15

PART C

5. (a) Derive the Barkhausen Criterion. Discuss the working of Hartley's and Colpitt's Oscillators. 15
- (b) What are the various properties of negative feedback ? Discuss in detail. What are the various topologies of feedback amplifiers ? Discuss their characteristics. 15
6. (a) What is a transistor ? Discuss its construction and operation. What are the various operating modes of BJT ? What are the various configurations of BJT ? Explain, their characteristics and applications. 15

- (b) What are multivibrators ? What are the various types of multivibrators ? Discuss the working and application of each. 15

PART D

7. (a) Discuss the classification of D.C. motor. Also, explain the characteristics of each type clearly, indicating their application area. 15
- (b) What is a transformer ? What are the basic functions performed by a transformer ? Explain the characteristics of an ideal transformer. Draw the phasor diagram of a step-down real transformer connected to a capacitive load. 15

- b. (a) A 4-pole, 3-phase, 440 V, 50 Hz induction motor has the following parameters for its circuit model (referred to the stator side on equivalent star basis).

$$r_1 = 1.1 \, \Omega, \quad x_1 = 1.12 \, \Omega, \quad r'_2 = 0.4 \, \Omega, \quad x'_2 = 1.12 \, \Omega, \quad x_m = 32 \, \Omega.$$

Rotational losses are 750 W.

- (i) For a speed of 1440 rpm, calculate the input current, power factor, net mechanical power, torque and efficiency.
- (ii) Calculate the maximum torque and the slip at which it occurs.

(b) Compare the following :

(i) Generator and Motor;

(ii) Two winding Transformer and Auto
Transformer;

(iii) Transformer and Induction Machine. 15