

This question paper contains 7 printed pages]

HPAS (Main)—2013

ELECTRICAL ENGINEERING

Paper I

Time : 3 Hours

Maximum Marks : 150

Note :— Attempt *Five* questions in all, taking at least *one* question from each Part.

Part A

1. (a) Find the Thevenin equivalent circuit for the network shown in Fig. 1 at terminal A-B : 15

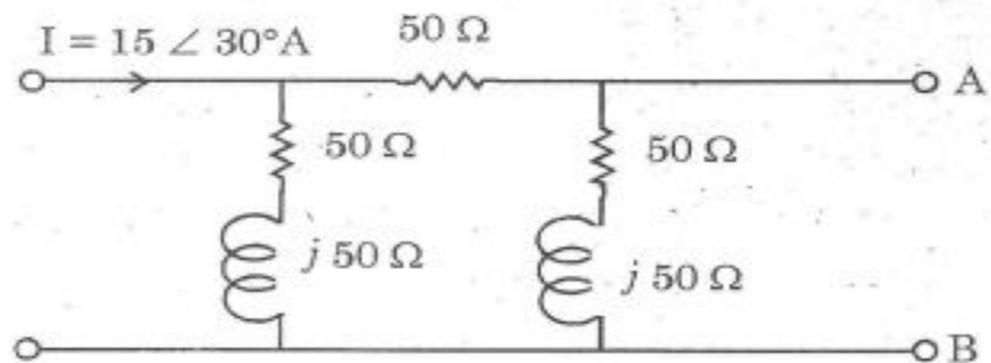


Fig. 1

P.T.O.

- (b) Write the restriction on the location of poles and zeros in the s -plane if a network function is :

15

$$F(s) = \frac{N(s)}{D(s)}$$

2. (a) Write the properties of RC impedance and R-L admittance functions, also explain its properties.

15

- (b) Synthesize the following function using Cauer form-I and Cauer form-II :

15

$$F(s) = \frac{3(s+2)(s+4)}{s(s+3)}$$

Part B

3. (a) Explain, what is meant by the transmission (ABCD) parameters of a two-port network. Derive the condition necessary to be satisfied for the

network to be :

16

(i) reciprocal

(ii) symmetrical

- (b) Find the trigonometric Fourier series for the half wave rectified sine wave shown in Fig. 2 and sketch the spectrum : 14

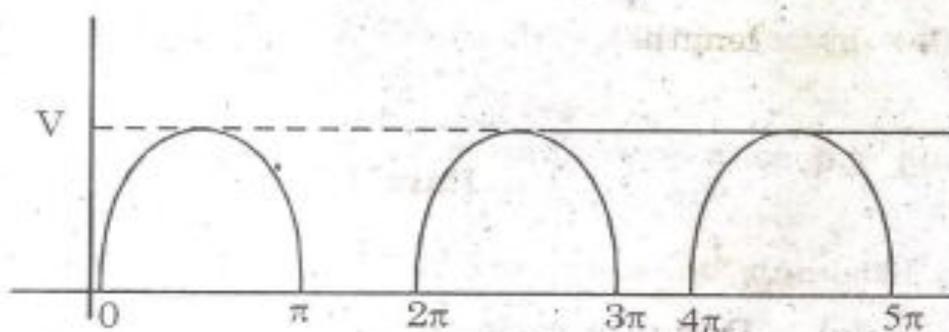


Fig. 2

4. (a) Given that $J = 10^3(x^2 + y^2)a$, A/m^2 , determine :
- (i) The current density at $(-3, 4, 6)$
- (ii) The rate of increase in the volume charge density at $(1, -2, 3)$

P.T.O.

- (iii) The current crossing a disk of radius 5 mm placed on the xy -plane and centred at the origin. 20

- (b) Show that in a good conductor, the skin depth δ is always much shorter than the wave length. 10

Part C

5. (a) Design a cycle counter that will output states 0 through 5. 10

- (b) Reduce the following Boolean expression : 10

(i) $(AB + C)(AB + D)$

(ii) $(\overline{A + \overline{BC}})(A\overline{B} + \overline{ABC})$

- (c) Which type of FF can receive slow rise times and fall times on the clock input ? 10
6. (a) Explain the principle of operation of : 14
- (i) Shaded pole motor
 - (ii) Stepper motor.
- (b) A three-phase, four-pole, star-connected 440 V induction motor has rotor resistance per phase = 0.1Ω and rotor reactance at standstill per phase = 0.8Ω . The ratio of stator turns per phase to rotor turns per phase = 1.3. Calculate :
- (i) The speed at which the mechanical power from the rotor will be maximum and
 - (ii) The maximum power from the motor. 16

Part D

7. (a) What are the advantages and disadvantages of one quadrant converters over two quadrant converters ? 14
- (b) Define the terms : 16
- (i) Frequency deviation of FM signal.
 - (ii) Deviation sensitivity
 - (iii) Deviation ratio
 - (iv) Carrier swing.
8. (a) What is meant by Gaussian noise ? What is the maximum power available from a noisy resistor R at a temperature T ? 10
- (b) Draw protective circuit for a thyristor against :
(i) High voltage
(ii) High current
with brief description of each one. 10

(c) Discuss the following :

(i) What happens if sampling rate exceeds Nyquist rate ?

(ii) What happens if sampling rate is less than Nyquist rate ?

10