

This question paper contains 8 printed pages]

HPAS (M)—2014

ELECTRICAL ENGINEERING

Paper I

Time : 3 Hours

Maximum Marks : 150

Note :— Attempt Five questions in all, taking at least one from each Part. Question No. 1 is compulsory.

Part A

1. (a) In transmission line analysis why do we use the concept of distributed elements ? 30
- (b) What are the demerits of a linear power supply ?
- (c) What is the drawback of an emitter feedback bias ?

P.T.O.

- (d) What is third approximation of a diode ?
- (e) State the two rule-of-thumb relations between size of a dynamo and the speed at which it is operated.

(a) Explain why a circularly polarized wave can still be plane wave. 14

(b) Show that :

$$E(x, t) = f_1(x - ct) + f_2(x + ct)$$

is solution of the wave equation

$$(\nabla^2 + \omega^2 \mu \epsilon)E = 0$$

with $k = \omega \sqrt{\mu \epsilon}$ and $c = \omega/k$.

Part B

3. (a) Place on a truth table and map the

function :

12

$$R = \overline{A}\overline{B}C\overline{D} + \overline{A}B\overline{C}\overline{D} + ABCD.$$

(b) Convert the following :

18

(i) Binary numbers to octal

11001, 10011101, 111010111

(ii) Decimal numbers to 10-bit binary

37.31, 6.215, 33.333.

P.T.O. —

4. (a) Draw a diagram showing the dark-lamp method of synchronization of two single-phase alternators and explain the conditions under

which :

16

- (i) The lamps will always remain dark.
- (ii) The lamps will always remain bright.
- (iii) The lamps will flicker in unison.

- (b) Explain why all field coils placed on field poles

have the same number of turns/pole and are

always connected in series.

14

Part C

5. (a) Write the Tellegen's theorem statement. Also, verify Tellegen's theorem for the network shown in Fig. 1 :

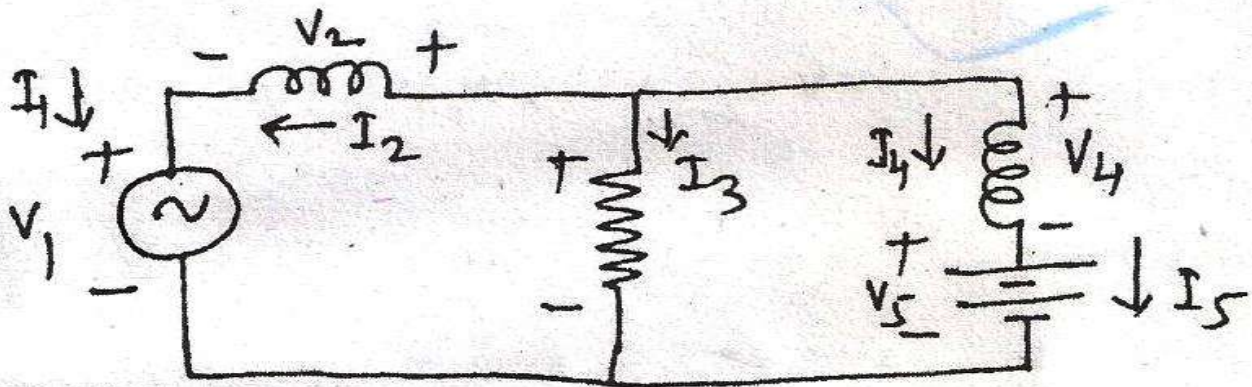


Fig. 1

Given $V_1 = 4 \text{ V}$, $V_2 = -2 \text{ V}$, $V_3 = 2 \text{ V}$,
 $V_4 = 8 \text{ V}$, $V_5 = -6 \text{ V}$ and $I_1 = 2 \text{ A}$, $I_2 = 2 \text{ A}$,
 $I_3 = -6 \text{ A}$, $I_4 = 4 \text{ A}$, $I_5 = 4 \text{ A}$.

- (b) Write necessary conditions for transfer functions.

14

P.T.O.

6. (a) A 10 kVA, 60 Hz, 4800/240 V transformer is tested by the open circuit and short circuit test.

The test data are as follows : 16

Test	V	A	W	Side used
Open Circuit	240	1.5	160	LV
Short Circuit	180	2.08	180	HV

Calculate, from these test data :

- (i) Equivalent resistance and reactance referred to HV side.
- (ii) Equivalent resistance and reactance referred to LV side.

- (b) Is it possible for a 60 Hz transformer to operate on 400 Hz ? Under what conditions ? 14

Part D

7. (a) Derive the relationship between total transmitted power and carrier power of AM signal. Calculate its transmission power efficiency. 15
- (b) A white noise of magnitude $\eta = 0.001 \mu\text{W/Hz}$ is applied to an RC low-pass filter of $R = 1 \text{ k}\Omega$ and $C = 0.1 \mu\text{F}$. Determine its cut-off frequency and the output noise power. 15
8. (a) A three-phase bridge inverter is fed from a 480 V dc source. The inverter operates in 180° conduction mode and it supplies a purely resistive, star connected load with $R = 10\Omega/\text{phase}$.

P.T.O.

Determine :

15

- (i) The rms value of load current
- (ii) The rms value of switch current
- (iii) The power delivered to the load, and
- (iv) The average source current.

(b) Briefly explain the following :

15

- (i) In what respect an IGBT is better than a MOSFET ?
- (ii) Working of Single-phase gate-commutation device current source inverter.